

1. Find the current I in the circuit shown Fig. 1.

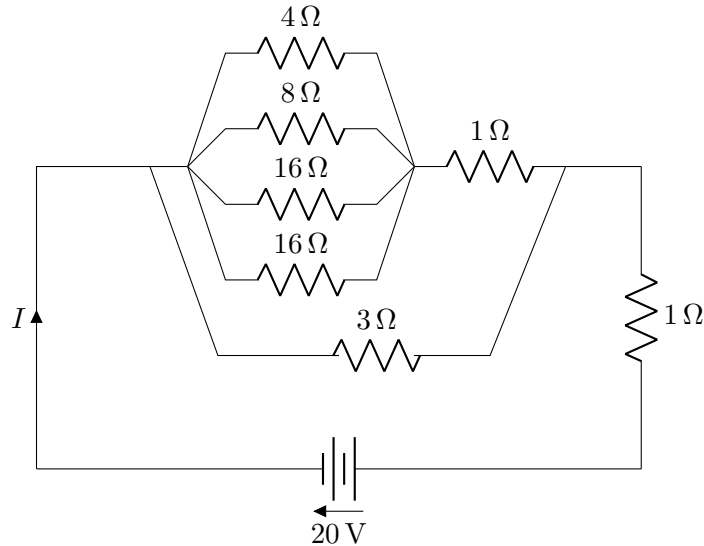


Figure 1: Problem 1.

2. In the circuit shown in Fig. 2, the power produced by bulb₁ and bulb₂ is 1 kW and 50 W, respectively. Which light has the higher resistance? (Assume the resistance of the light bulb remains constant with time.)

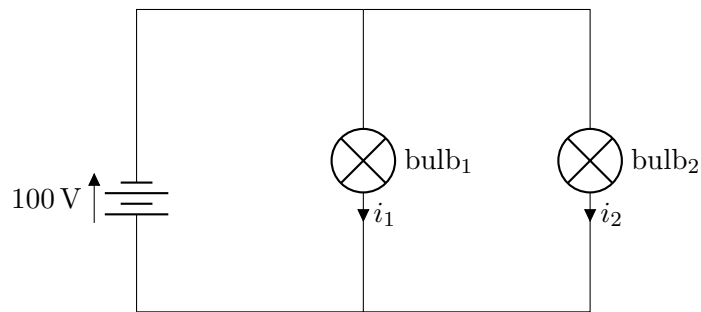


Figure 2: Problem 2.

3. A regular tetrahedron is a pyramid with a triangular base. Six $R = 10.0 \Omega$ resistors are placed along its six edges, with junctions at its four vertices, as shown in Fig. 3. A 12.0-V battery is connected to any two of the vertices. Find (i) the equivalent resistance of the tetrahedron between these vertices and (ii) the current in the battery.

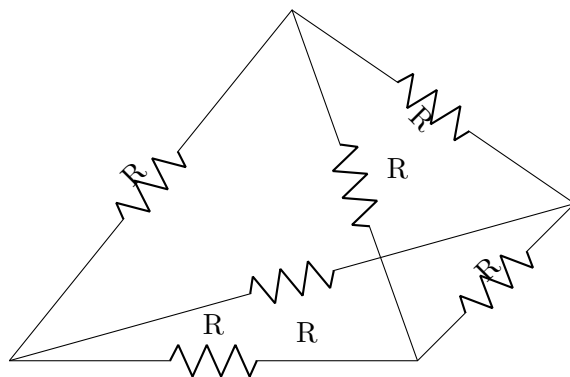


Figure 3: Problem 3.

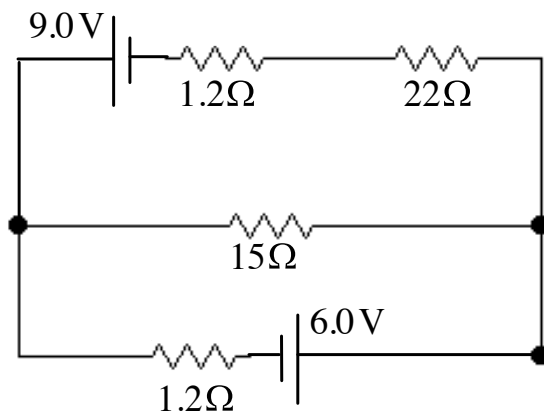


Figure 4: Problem 4.

4. Determine the magnitude and directions of the currents through $R_1 = 22 \Omega$ and $R_2 = 15 \Omega$ in the circuit of Fig. 4. The batteries have an internal resistance of $r = 1.2 \Omega$.

5. Determine the magnitude and directions of the currents in each resistor shown in Fig. 5. The batteries has emfs of $\varepsilon_1 = 9 \text{ V}$ and $\varepsilon_2 = 12 \text{ V}$ and the resistors have values of $R_1 = 25 \Omega$, $R_2 = 18 \Omega$, and $R_3 = 35 \Omega$.

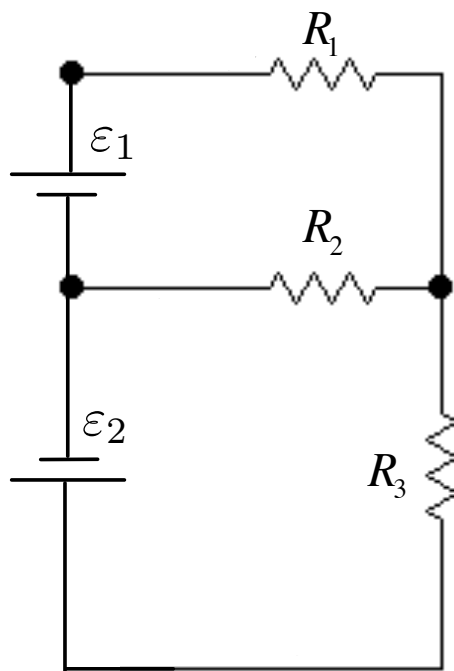


Figure 5: Problem 5.